



# INDIAN INSTITUTE OF TECHNOLOGY, ROPAR

## PROJECT PRESENTATION (CP-302)

**A Configurable Direct Digital Frequency Synthesizer Based on LUT and Rotation: Reproduction and Custom Hardware Implementation Using Verilog and Python-Based Simulation**

**SUBMITTED TO :**

Dr. Devarshi Das

Dr. Neeraj Goel

**SUBMITTED BY :**

Amitoj Singh

2022EEB1295

# Abstract

- Reproduced the DDFS architecture from IEEE TCAS-I 2019.
- Implemented using Verilog HDL with modular hierarchy.
- Simulated sinusoidal outputs using Python.
- Verified performance metrics: frequency output, SFDR.

# Introduction

DDFS: Key for radar, comms, and agile RF systems.

Paper proposes LUT + Rotation (LUT-ROT) based DDFS.

Highlights:

- Multi-Bit Rotation Tree (MBRT)
- Mode-configurable operation
- High SFDR, low power

 


Fig. 1 - Conventional DDFS architecture [1]

# Reference paper summary

**Hybrid LUT + Rotation:** Reduced ROM + latency.

**MBRT:** Low power, short pipeline.

**Modes:** Tunable trade-offs (speed vs power).

Achieved:

- 102-dBc SFDR
- 2.2-GHz frequency
- 6.9 mW/GHz efficiency

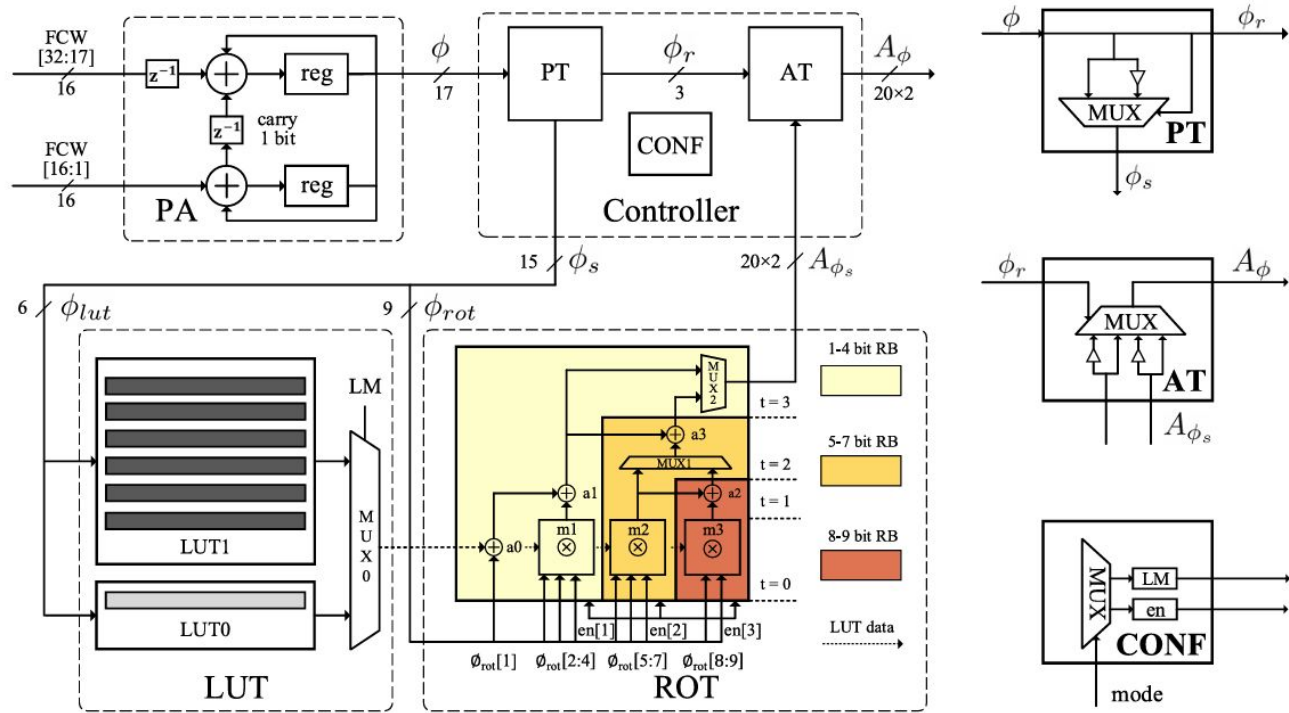


Fig. 2 - Final proposed circuit implementations [1]

$\phi_r$	$\phi \Rightarrow \phi_s$	$A_{\phi_s} \Rightarrow A_\phi$
000	$\phi [4:N]$	$(\cos \frac{\pi}{4} \phi_s, \sin \frac{\pi}{4} \phi_s)$
001	$\sim \phi [4:N]$	$(\sin \frac{\pi}{4} \phi_s, \cos \frac{\pi}{4} \phi_s)$
010	$\phi [4:N]$	$(-\sin \frac{\pi}{4} \phi_s, \cos \frac{\pi}{4} \phi_s)$
011	$\sim \phi [4:N]$	$(-\cos \frac{\pi}{4} \phi_s, \sin \frac{\pi}{4} \phi_s)$
100	$\phi [4:N]$	$(-\cos \frac{\pi}{4} \phi_s, -\sin \frac{\pi}{4} \phi_s)$
101	$\sim \phi [4:N]$	$(-\sin \frac{\pi}{4} \phi_s, -\cos \frac{\pi}{4} \phi_s)$
110	$\phi [4:N]$	$(\sin \frac{\pi}{4} \phi_s, -\cos \frac{\pi}{4} \phi_s)$
111	$\sim \phi [4:N]$	$(\cos \frac{\pi}{4} \phi_s, -\sin \frac{\pi}{4} \phi_s)$

Fig. 3 - Phase and Amplitude transformations [1]

# Verilog Implementation Review

**PA\_16bit.v:** 32-bit phase accumulator (pipelined).

**lut.v:** ROM with xc, yc, xp, yp values (Python-generated).

**rot\_new.v:** MBRT rotation logic.

**PT\_transformed.v / at.v:**  $\pi/4$  symmetry transforms.

**conf.v:** Mode and block enable controls.

**top.v / top\_tb.v:** System integration and testbench.

## PHASE ACCUMULATOR

```
1 module phase_accumulator_16bit_pipelined(  
2     input wire clk,  
3     input wire rst,  
4     input wire [31:0] FCW,  
5     output reg [31:0] phase  
6 );  
7  
8     wire [15:0] FCW_lower = FCW[15:0];  
9     wire [15:0] FCW_upper = FCW[31:16];  
10  
11     reg [15:0] phase_lower;  
12     reg [15:0] phase_upper;  
13  
14     wire carry;  
15  
16     always @(posedge clk or posedge rst) begin  
17         if (rst)  
18             phase_lower <= 16'b0;  
19         else  
20             phase_lower <= phase_lower + FCW_lower;  
21     end  
22  
23     assign carry = (phase_lower + FCW_lower < phase_lower) ? 1'b1 : 1'b0;  
24  
25     always @(posedge clk or posedge rst) begin  
26         if (rst)  
27             phase_upper <= 16'b0;  
28         else  
29             phase_upper <= phase_upper + FCW_upper + carry;  
30             phase <= {phase_upper, phase_lower};  
31     end  
32  
33 endmodule
```

## PHASE TRANSFORMER

```
1 module PT #(  
2     parameter n = 18,  
3     parameter l = 6  
4 )(  
5     input wire [31:0] PA_out,  
6     output wire [2:0] phi_r,  
7     output wire [l-1:0] phi_lut,  
8     output wire [n-4-l:0] phi_rot  
9 );  
10  
11     wire [n-1:0] phi;  
12     assign phi = PA_out[31 -: n];  
13  
14     wire [n-4:0] phi_s_raw;  
15     assign phi_r = phi[n-1 -: 3];  
16     assign phi_s_raw = phi[n-4:0];  
17  
18     wire [n-4:0] phi_s_transformed;  
19  
20     assign phi_s_transformed = (phi_r[0] == 1'b0) ? phi_s_raw : ~phi_s_raw;  
21  
22     assign phi_lut = phi_s_transformed[n-4 -: l];  
23     assign phi_rot = phi_s_transformed[n-4-l:0];  
24  
25 endmodule
```



# LUT

```
1 module LUT_ROM #(
2     parameter n = 18,
3     parameter l = 6
4 )
5     input wire [l-1:0] phi_lut,
6     input wire      LM,
7     output wire [63:0] lut_data
8 );
9
10    wire [3:0] addr_lut0 = phi_lut[l-1 -: 4];
11    wire [5:0] addr_lut1 = phi_lut;
12
13    reg [63:0] ROM0 [0:15];
14    reg [63:0] ROM1 [0:63];
15
16    reg [63:0] data_out;
17
18    initial begin
19        ROM0[ 0] = 64'h8000000000648000;
20        ROM0[ 1] = 64'h7FD3106B2F646054;
21        ROM0[ 2] = 64'h7F4C80D6136400A8;
22        ROM0[ 3] = 64'h7E6C9140616350FC;
23        ROM0[ 4] = 64'h7D33F1A9CE62514E;
24        ROM0[ 5] = 64'h7BA37212106121A0;
25        ROM0[ 6] = 64'h79BC4278DE5FA1F1;
26        ROM0[ 7] = 64'h777F92DDF05DE240;
27        ROM0[ 8] = 64'h74EF1340FF5BD28E;
28        ROM0[ 9] = 64'h720C83A1C65992DA;
29        ROM0[10] = 64'h6ED9F40000571324;
30        ROM0[11] = 64'h6B59945B6C54536C;
31        ROM0[12] = 64'h678DE4B3C95153B1;
32        ROM0[13] = 64'h63798508D94E23F4;
33        ROM0[14] = 64'h5F1F655A614AB434;
34        ROM0[15] = 64'h5A8285A828471471;
35
36    end
```

```
106     always @(*) begin
107         case (LM)
108             1'b0: data_out = ROM0[addr_lut0];
109             1'b1: data_out = ROM1[addr_lut1];
110             default: data_out = 64'b0;
111         endcase
112     end
113
114     assign lut_data = data_out;
115
116 endmodule
117
```

# ROT

```
module MBRT_ROT [
    input wire      clk,          // clock
    input wire      rst,          // synchronous reset
    input wire [2:0] en,          // enable signals for stages [en0,en1,en2]
    input wire [8:0] phi_rot,     // 9-bit rotation word (partitioned into 3 segments)
    input wire signed [63:0] lut_data,
    output reg signed [19:0] xs,   // 20-bit signed output X = xc + rotated_offset_x
    output reg signed [19:0] ys   // 20-bit signed output Y = yc + rotated_offset_y
];

    wire signed [19:0] xc = lut_data[63:44]; // 20-bit signed coarse X (MSB int, rest frac)
    wire signed [19:0] yc = lut_data[43:24]; // 20-bit signed coarse Y
    wire signed [11:0] xp = lut_data[23:12]; // 12-bit signed fine X (to be rotated)
    wire signed [11:0] yp = lut_data[11:0];  // 12-bit signed fine Y

    // Sign-extend 12-bit inputs to 20-bit fixed-point (MSB rep.)
    wire signed [19:0] x0_ext = { 8'b0, xp };
    wire signed [19:0] y0_ext = { 8'b0, yp };

    // Partition phi_rot into three 3-bit signed segments for the stages
    wire signed [2:0] phi0 = phi_rot[2:0]; // stage 0 angle bits
    wire signed [2:0] phi1 = phi_rot[5:3]; // stage 1 angle bits
    wire signed [2:0] phi2 = phi_rot[8:6]; // stage 2 angle bits

    // Pipeline registers for intermediate X,Y values at each stage
    reg signed [19:0] stage1_x, stage1_y;
    reg signed [19:0] stage2_x, stage2_y;
    reg signed [19:0] stage3_x, stage3_y;

    always @(posedge clk) begin
        if (rst) begin
            stage1_x <= 20'b0;
            stage1_y <= 20'b0;
            stage2_x <= 20'b0;
            stage2_y <= 20'b0;
            stage3_x <= 20'b0;
        end
    end
```

```
always @(posedge clk) begin
    if (rst) begin
        stage1_x <= 20'b0;
        stage1_y <= 20'b0;
        stage2_x <= 20'b0;
        stage2_y <= 20'b0;
        stage3_x <= 20'b0;
        stage3_y <= 20'b0;
        xs <= 20'b0;
        ys <= 20'b0;
    end else begin
        // Stage 0 (first 3-bit rotation)
        if (en[0]) begin
            // Fixed-point multiply-add for rotation: shift right by 3 after multiply
            // dx0 = x0_ext * phi0 / 8; dy0 = y0_ext * phi0 / 8;
            // Then x1 = x0_ext - dy0; y1 = y0_ext + dx0;
            stage1_x <= xc - ( (x0_ext * phi0) >>> 6 );
            stage1_y <= yc + ( (y0_ext * phi0) >>> 6 );
        end else begin
            // Bypass this stage
            stage1_x <= x0_ext;
            stage1_y <= y0_ext;
        end

        // Stage 1 (second 3-bit rotation)
        if (en[1]) begin
            stage2_x <= stage1_x - ( (x0_ext * phi1) >>> 9 );
            stage2_y <= stage1_y + ( (y0_ext * phi1) >>> 9 );
        end else begin
            stage2_x <= stage1_x;
            stage2_y <= stage1_y;
        end

        // Stage 2 (third 3-bit rotation)
        if (en[2]) begin
            stage3_x <= stage2_x - ( (x0_ext * phi2) >>> 12 );
            stage3_y <= stage2_y + ( (y0_ext * phi2) >>> 12 );
        end else begin
            stage3_x <= stage2_x;
            stage3_y <= stage2_y;
        end

        xs <= stage3_x;
        ys <= stage3_y;
    end
end
```

## ROT

```
// Stage 2 (third 3-bit rotation)
if (en[2]) begin
    stage3_x <= stage2_x - ( (x0_ext * phi2) >>> 12 );
    stage3_y <= stage2_y + ( (y0_ext * phi2) >>> 12 );
end else begin
    stage3_x <= stage2_x;
    stage3_y <= stage2_y;
end

// Final outputs: add coarse (xc,yc) to the rotated offset
xs <= stage3_x;
ys <= stage3_y;

end
endmodule
```

## AMPLITUDE TRANSFORMER

```
module AT_block(
    input wire [2:0] phi_r,
    input wire signed [19:0] xs, ys, // first-octant cosine (xs) and sine (ys)
    output reg signed [19:0] sin_out, cos_out
);

// Intermediate shifted versions with sign bit zeroed
wire [18:0] xs_shifted = xs[19:1];
wire [18:0] ys_shifted = ys[19:1];

// Function to apply sign manually (set MSB = 1 if negative)
function [19:0] make_signed;
    input [18:0] val;
    input sign; // 0 = positive, 1 = negative
    begin
        make_signed = {sign, val};
    end
endfunction

always @* begin
    case (phi_r)
        3'b000: begin sin_out = make_signed(ys_shifted, 1'b0); cos_out = make_signed(xs_shifted, 1'b0); end
        3'b001: begin sin_out = make_signed(xs_shifted, 1'b0); cos_out = make_signed(ys_shifted, 1'b0); end
        3'b010: begin sin_out = make_signed(xs_shifted, 1'b0); cos_out = make_signed(ys_shifted, 1'b1); end
        3'b011: begin sin_out = make_signed(ys_shifted, 1'b0); cos_out = make_signed(xs_shifted, 1'b1); end
        3'b100: begin sin_out = make_signed(ys_shifted, 1'b1); cos_out = make_signed(xs_shifted, 1'b1); end
        3'b101: begin sin_out = make_signed(xs_shifted, 1'b1); cos_out = make_signed(ys_shifted, 1'b1); end
        3'b110: begin sin_out = make_signed(xs_shifted, 1'b1); cos_out = make_signed(ys_shifted, 1'b0); end
        3'b111: begin sin_out = make_signed(ys_shifted, 1'b1); cos_out = make_signed(xs_shifted, 1'b0); end
        default: begin sin_out = 20'b0; cos_out = 20'b0; end
    endcase
end

endmodule
```

# CONF

```
module conf_block (  
    input        clk,  
    input        rst,  
    input [1:0]   mode,  
    output reg    LM,    // LUT mode: 1=LUT1, 0=LUT0  
    output reg [2:0] en,  // rotation block enables (en2,en1,en0)  
    output reg [3:0] L,   // number of MSBs for LUT (phi_lut bits)  
    output reg [3:0] R    // number of LSBs for rotation (phi_rot bits)  
);  
  
    // Decode mode into new control signals (before pipelining)  
    reg new_LM;  
    reg [2:0] new_en;  
    reg [3:0] new_L, new_R;  
    always @(*) begin  
        case (mode)  
            2'b00: begin new_LM = 1'b1; new_en = 3'b000; new_L = 4'd6; new_R = 4'd9; end  
            2'b01: begin new_LM = 1'b1; new_en = 3'b001; new_L = 4'd6; new_R = 4'd9; end  
            2'b10: begin new_LM = 1'b1; new_en = 3'b011; new_L = 4'd6; new_R = 4'd9; end  
            2'b11: begin new_LM = 1'b1; new_en = 3'b111; new_L = 4'd6; new_R = 4'd9; end  
            default: begin new_LM = 1'b1; new_en = 3'b000; new_L = 4'd9; new_R = 4'd0; end  
        endcase  
    end  
  
    // Pipeline registers (3-cycle delay) for control signals  
    reg LM_d0, LM_d1;  
    reg [2:0] en_d0, en_d1;  
    reg [3:0] L_d0, L_d1;  
    reg [3:0] R_d0, R_d1;  
    always @(posedge clk or posedge rst) begin  
        if (rst) begin  
            // On reset, clear all registers and outputs  
            LM      <= 1'b0;  
            en      <= 3'b000;  
            L       <= 4'd0;  
            R       <= 4'd0;  
            LM_d0   <= 1'b0; LM_d1 <= 1'b0;  
            en_d0   <= 3'b000; en_d1 <= 3'b000;  
            L_d0    <= 4'd0; L_d1  <= 4'd0;  
            R_d0    <= 4'd0; R_d1  <= 4'd0;  
        end  
        LM_d1 <= LM_d0;  
        en_d1 <= en_d0;  
        L_d1  <= L_d0;  
        R_d1  <= R_d0;  
        LM    <= LM_d1;  
        en    <= en_d1;  
        L     <= L_d1;  
        R     <= R_d1;  
    end  
endmodule
```

```
always @(posedge clk or posedge rst) begin  
    if (rst) begin  
        // On reset, clear all registers and outputs  
        LM      <= 1'b0;  
        en      <= 3'b000;  
        L       <= 4'd0;  
        R       <= 4'd0;  
        LM_d0   <= 1'b0; LM_d1 <= 1'b0;  
        en_d0   <= 3'b000; en_d1 <= 3'b000;  
        L_d0    <= 4'd0; L_d1  <= 4'd0;  
        R_d0    <= 4'd0; R_d1  <= 4'd0;  
    end else begin  
        // Stage 1: capture new config  
        LM_d0 <= new_LM;  
        en_d0 <= new_en;  
        L_d0  <= new_L;  
        R_d0  <= new_R;  
        // Stage 2  
        LM_d1 <= LM_d0;  
        en_d1 <= en_d0;  
        L_d1  <= L_d0;  
        R_d1  <= R_d0;  
        // Stage 3: output registers (final delayed signals)  
        LM    <= LM_d1;  
        en    <= en_d1;  
        L     <= L_d1;  
        R     <= R_d1;  
    end  
end  
endmodule
```



# TOP

```
> module top (...
);

// Internal phase accumulator output
wire [31:0] phase;          // full 32-bit phase from PA

// Phase transformation outputs
wire [2:0] phi_r;           // 3-bit quadrant indicator from PT
wire [5:0] phi_lut;         // 6-bit address for LUT (phi_lut bits)
wire [8:0] phi_rot;         // 9-bit rotation word (phi_rot bits)

// LUT output
wire [63:0] lut_data;       // 64-bit packed sine/cosine data from LUT

// Rotation block outputs
wire signed [19:0] xs;      // 20-bit rotated sine (coarse + offset)
wire signed [19:0] ys;      // 20-bit rotated cosine (coarse + offset)

// Configuration signals
wire      LM;               // LUT mode select (1=LUT1, 0=LUT0)
wire [2:0] en;              // enable signals for rotation stages [en0, en1, en2]
wire [3:0] L;               // number of MSBs for LUT (phi_lut width)
wire [3:0] R;               // number of LSBs for rotation (phi_rot width)

// Instantiate Phase Accumulator (PA)
// Accumulates FCW into 32-bit phase with two 16-bit pipelined accumulators
> phase_accumulator_16bit_pipelined PA_inst (...
);

// Instantiate Configuration block (CONF)
// Decodes mode into control signals for LUT/ROT partitioning
> conf_block CONF_inst (...
);

// Instantiate Phase Transformation (PT)
// Splits the phase into quadrant bits, LUT index, and rotation index
> PT #(...
```

```
> PT #(...
);

// Instantiate Look-Up Table (LUT)
// Selects sine/cosine values from ROM based on phi_lut and LM
> LUT_ROM LUT_inst (...
);

// Instantiate Rotation block (MBRT_ROT)
// Performs micro-rotation on LUT outputs using phi_rot and enable signals en[2:0]
> MBRT_ROT ROT_inst (...
);

// Instantiate Inverse Symmetry (AT_block)
// Maps the rotated outputs (xs, ys) to final sine/cosine outputs (sin_out, cos_out)
// based on the quadrant indicator phi_r
> AT_block AT_inst (...
);

endmodule
```

# Python LUT generator

Generated 64 samples from 0 to  $\pi/4$ .

Computed:

- $x_c = \cos(\theta), y_c = \sin(\theta)$
- $x_p = (\pi/4) \cdot \cos(\theta), y_p = (\pi/4) \cdot \sin(\theta)$

Scaled to fixed-point:

- $x_c, y_c \rightarrow 20\text{-bit}$
- $x_p, y_p \rightarrow 12\text{-bit}$

Exported to ROM for Verilog LUT.

# Simulation Results

FCW inputs tested using **top\_tb.v**.

Python:

- Converts output to float
- Plots sine/cos waveforms and smoothens them
- Performs FFT using smoothed values

Output frequency matched predictions:

- $f_{\text{out}} = (\text{FCW} \times f_{\text{clk}}) / 2^n$

Link to codes - [link](#)

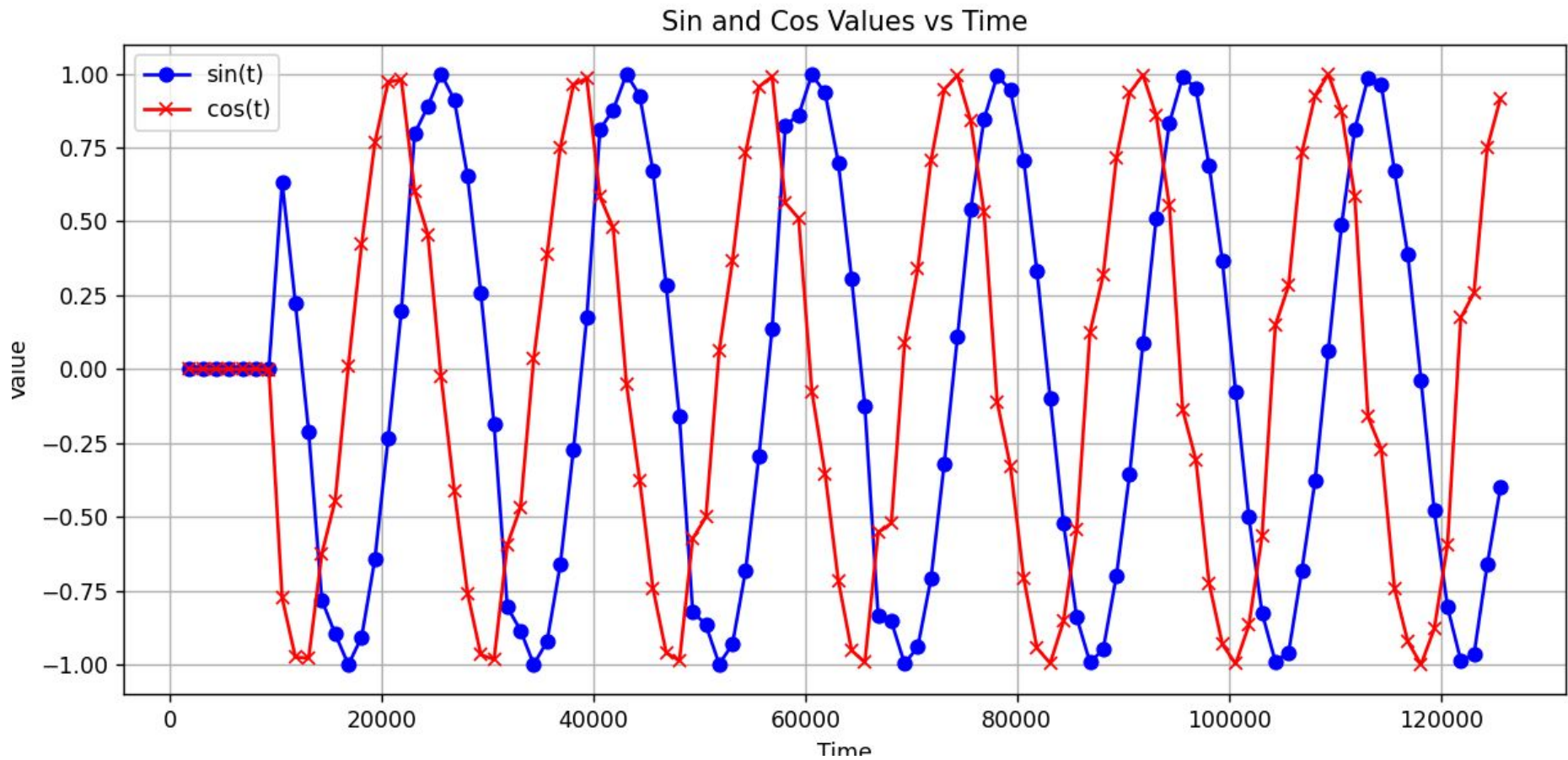


Fig. 4 - Output obtained



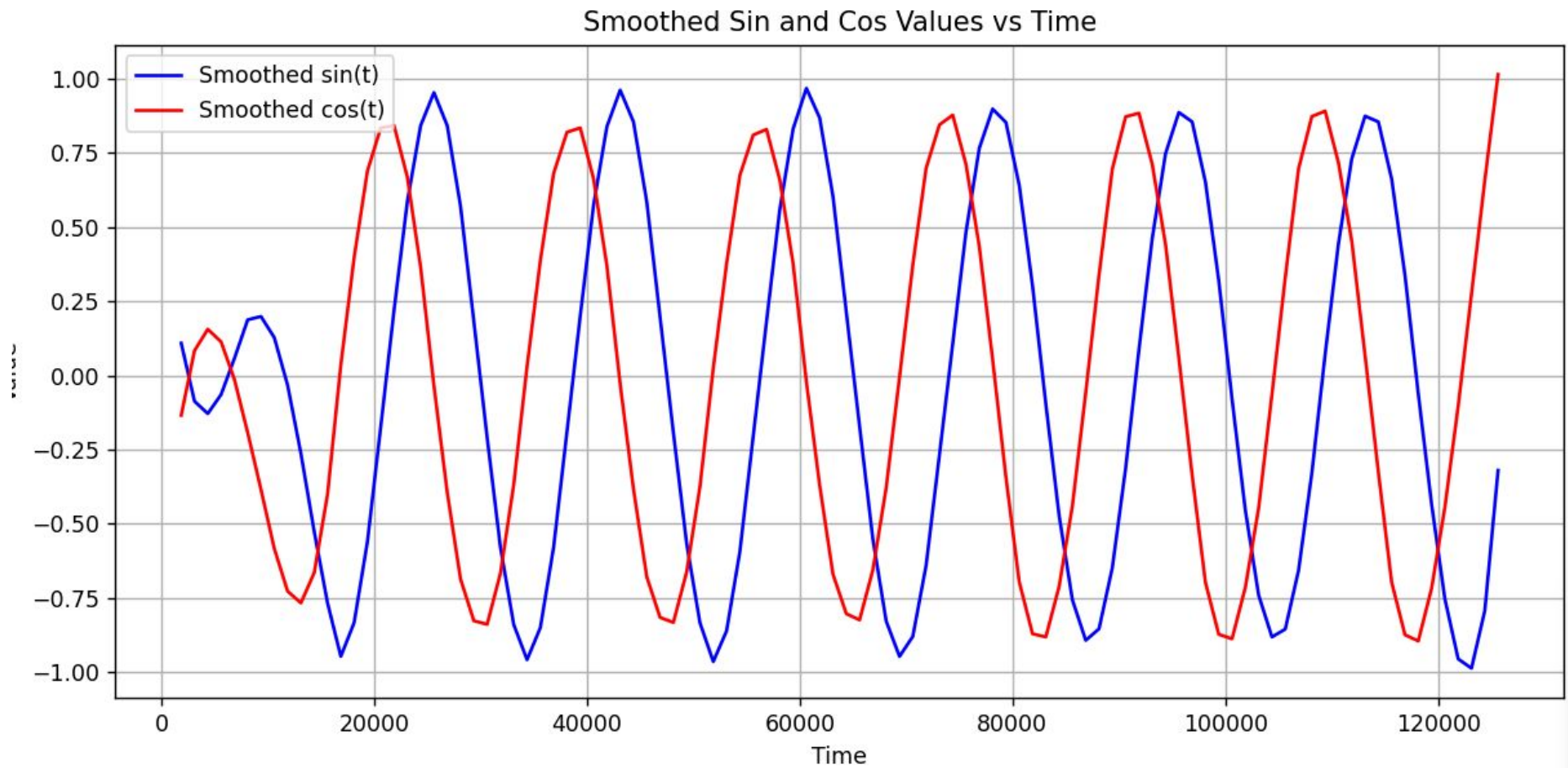


Fig. 5 - Output obtained

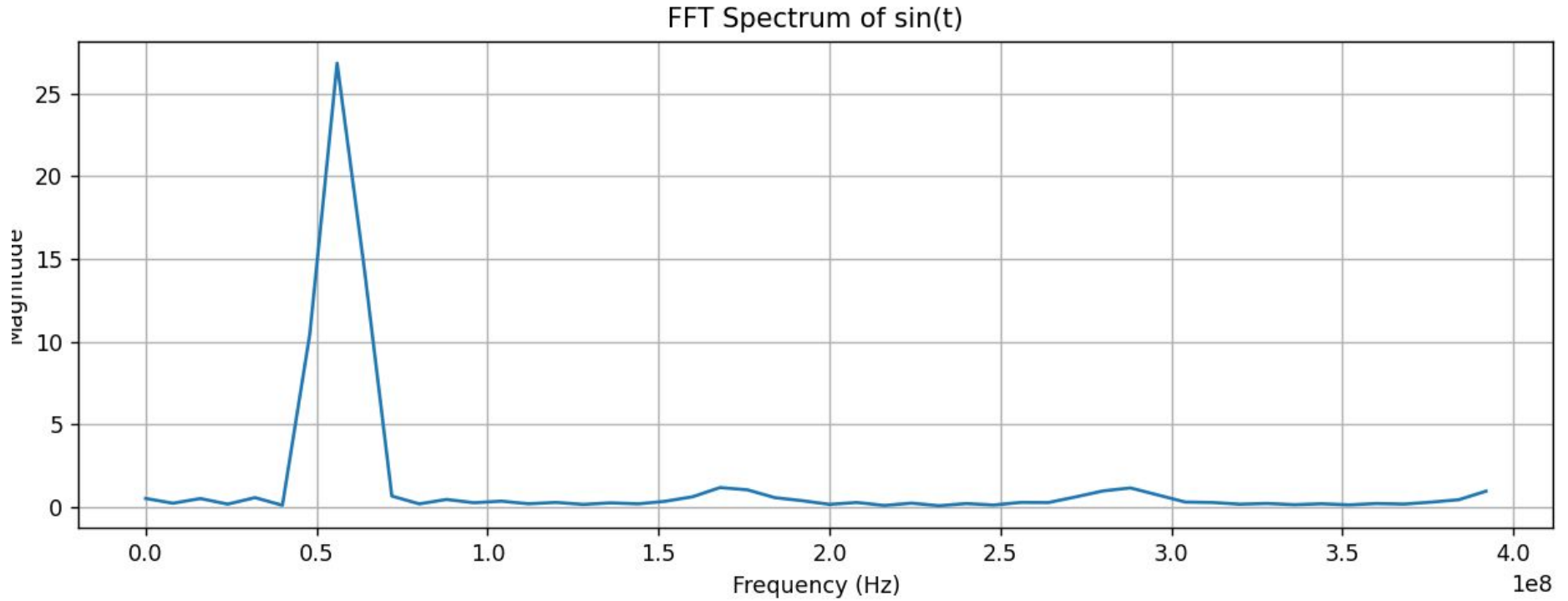


Fig. 6 - Output obtained

# Module Analysis

**PA\_16bit.v:** Pipelined accumulator (fast, low delay).

**lut.v:** Compact, fast amplitude lookup.

**rot\_new.v:** Tree-based rotation:

- $x_s = x_c - \varphi \cdot y_p$
- $y_s = y_c + \varphi \cdot x_p$

**PT\_transformed / at.v:** Angle compression logic.

**conf.v:** Dynamic mode and LUT control.

# Discussions

Output frequency accurate; SFDR lower than expected.

Potential reasons:

- Lower LUT precision
- Approximation in rotation
- FFT resolution limits

Strength: Successfully mimics architecture at lower scale.

# Future Work

Use BRAMs for LUTs.

Enhance bit resolution post-PA.

Vary FCW to study SFDR trends.

FPGA + DAC implementation.

Optimize area, power, and speed.

# Conclusion

- Reproduced LUT-ROT DDFS architecture.
- Verified correct frequency synthesis.
- Shows potential for custom RF synthesizer design.

# References

[1] Yang et al., *"A 2.2-GHz Configurable Direct Digital Frequency Synthesizer Based on LUT and Rotation,"* IEEE TCAS-I, 2019.

**Thank you!**